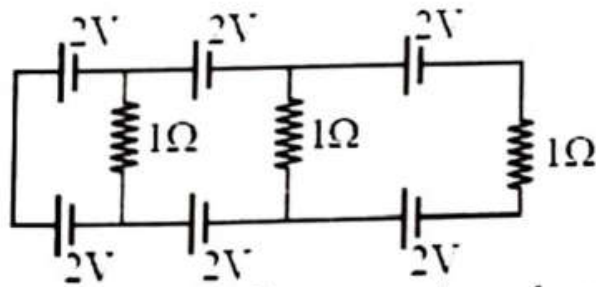


Q 02



In the above circuit the current in each resistance is [2017]

- (a) 0.5A (b) 0 A (c) 1 A (d) 0.25 A

answer

(b) The potential difference in each loop is zero.
 \therefore No current will flow or current in each resistance is Zero.