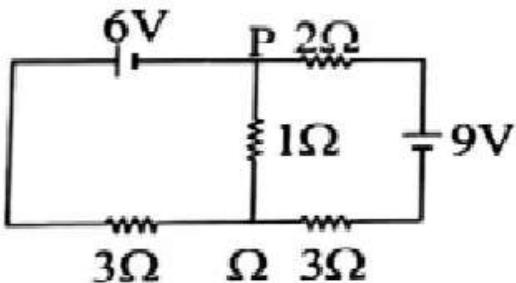


**Q 03** In the circuit shown, the current in the  $1\Omega$  resistor is : [2015]




- (a) 0.13 A, from Q to P      (b) 0.13 A, from P to Q  
 (c) 1.3A from P to Q      (d) 0A

**solution**

(a) From KVL


$$-6 + 3I_1 + 1(I_1 - I_2) = 0$$

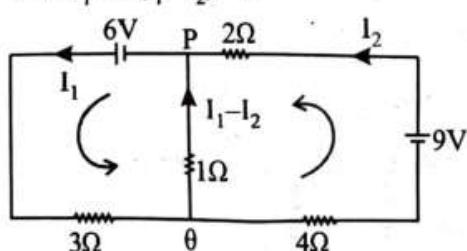

$$E_{eq} = \frac{E_1 + E_2}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{\frac{6}{3} + \frac{9}{5}}{\frac{1}{3} + \frac{1}{5}} = \frac{3}{8} \text{ V}$$

$$\therefore I = \frac{E_{eq}}{R_{eq}} = \frac{3}{\frac{15}{8} + 1} = \frac{3}{23} = 0.13 \text{ A}$$

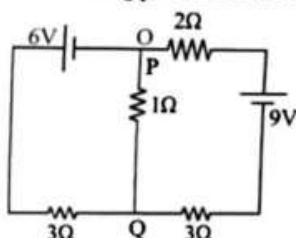Considering potential at P as 0V and at Q as x volt, then



$$\frac{x-6}{3} + \frac{x-0}{1} + \frac{x+9}{5} = 0$$

$$\therefore x = \frac{2}{23}$$

$$\therefore i = \frac{x-0}{1} = \frac{2}{23} = 0.13 \text{ A}$$

From O to P

