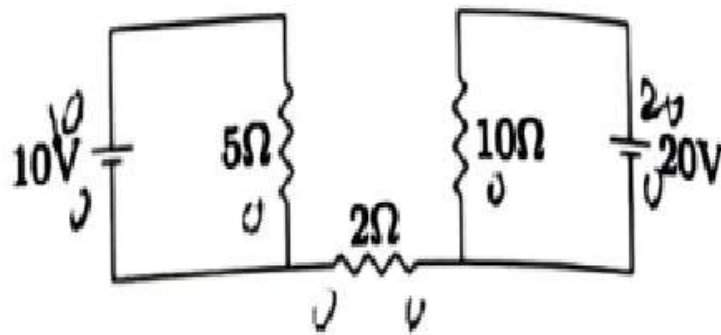


Q 05

Find out the value of current through $2\ \Omega$ resistance for the given circuit.
(2005)



- (A) 5 A (B) 2 A (C) zero (D) 4 A

Sol. Kirchhoff's junction law prohibits current flow through $2\ \Omega$ resistance.

Ans. C