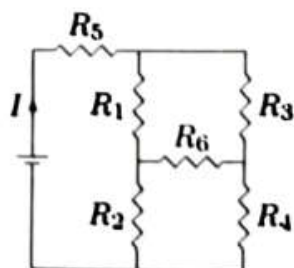


Q 06

In the given circuit, it is observed that the current I is independent of the value of the resistance R_6 . Then the resistance values must satisfy (2001)



- (A) $R_1 R_2 R_5 = R_3 R_4 R_6$
 (B) $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$
 (C) $R_1 R_4 = R_2 R_3$
 (D) $R_1 R_3 = R_2 R_4$

Sol. Effective resistance of the circuit depends on R_6 unless Wheatstone bridge formed by R_1, R_2, R_3, R_4 and R_6 is balanced. Thus, the current becomes independent of R_6 only when the bridge is balanced i.e., $R_1/R_2 = R_3/R_4$. It might be tedious but worth to find the current I in terms of R_1, R_2, R_3, R_4, R_5 and R_6 and explicitly show the independence of I in the balanced condition. *Hint:* Use Kirchhoff's law in the three loops and solve for I .

Ans. C \square