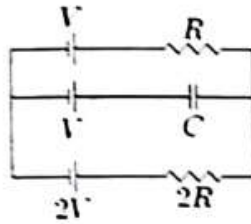



# Q 07

In the given circuit, with steady current, the potential difference across the capacitor must be (2001)



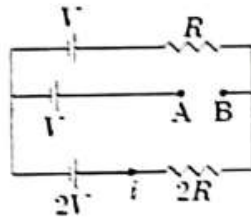- (A)  $V$  (B)  $V/2$  (C)  $V/3$  (D)  $2V/3$

**Sol.** In the steady state, a capacitor acts like an open circuit element (see figure).



Apply Kirchhoff's loop law to get

$$2V - 2iR - iR - V = 0.$$

which gives the current  $i = V/(3R)$ . Traversing from B to A through the upper branch gives the potential of A w.r.t. potential of B as

$$V_A = V_B - iR - V + V = V_B - V/3.$$

Ans. C  $\square$