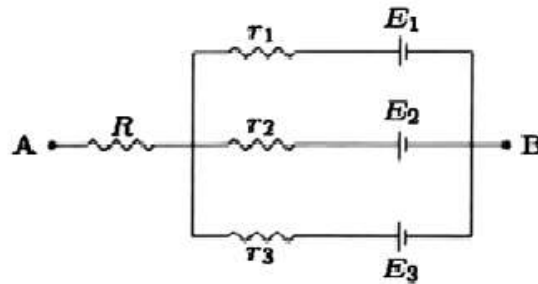



Q 10

In the circuit shown in figure $E_1 = 3\text{ V}$, $E_2 = 2\text{ V}$, $E_3 = 1\text{ V}$ and $R = r_1 = r_2 = r_3 = 1\ \Omega$. (1981)



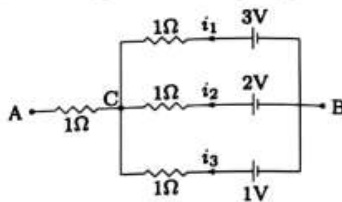- (a) Find the potential difference between the points A and B and the currents through each branch.
 (b) If r_2 is short circuited and the point A is connected to point B , find the currents through E_1 , E_2 , E_3 and the resistor R .

Sol. Let i_1 , i_2 , and i_3 be the currents through the batteries $E_1 = 3\text{ V}$, $E_2 = 2\text{ V}$, $E_3 = 1\text{ V}$, respectively.



There is no current through $R = 1\ \Omega$. Apply Kirchhoff's junction law at node C to get

$$i_1 + i_2 + i_3 = 0. \quad (1)$$


Apply Kirchhoff's loop law in the upper and lower loops, to get

$$3 - i_1 + i_2 - 2 = 0, \quad (2)$$

$$2 - i_2 + i_3 - 1 = 0. \quad (3)$$

Solve equations (1)–(3) to get $i_1 = 1\text{ A}$, $i_2 = 0\text{ A}$, and $i_3 = -1\text{ A}$. Since $i_2 = 0\text{ A}$ and current through R is zero, $V_{AB} = V_{CB} = E_2 = 2\text{ V}$.

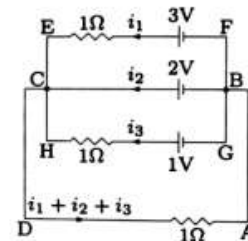The circuit after shorting $r_2 = 1\ \Omega$ and connecting point A to B is shown in the figure.



Apply Kirchhoff's loop law in loops $ABCDA$, $FECBF$, and $BCHGB$ to get

$$2 - (i_1 + i_2 + i_3) = 0, \quad (4)$$

$$3 - i_1 - 2 = 0, \quad (5)$$

$$2 + i_3 - 1 = 0. \quad (6)$$

Solve equations (4)–(6) to get $i_1 = 1\text{ A}$, $i_2 = 2\text{ A}$, and $i_3 = -1\text{ A}$. The current through the resistor R is $i_1 + i_2 + i_3 = 1 + 2 - 1 = 2\text{ A}$.

Ans. (a) 2 V , 1 A , 0 , -1 A (b) 1 A , 2 A , -1 A , 2 A □