


Q. 02

Let there be n resistors R_1, \dots, R_n with $R_{\max} = \max(R_1, \dots, R_n)$ and $R_{\min} = \min\{R_1, \dots, R_n\}$. Show that when they are connected in parallel, the resultant resistance $R_p = R_{\min}$ and when they are connected in series, the resultant resistance $R_s > R_{\max}$. Interpret the result physically.


Solution:

Key concept: *Parallel grouping:* Same potential difference appeared across each resistance but current distributes in the reverse ratio of their

resistance, i.e. $i \propto \frac{1}{R}$

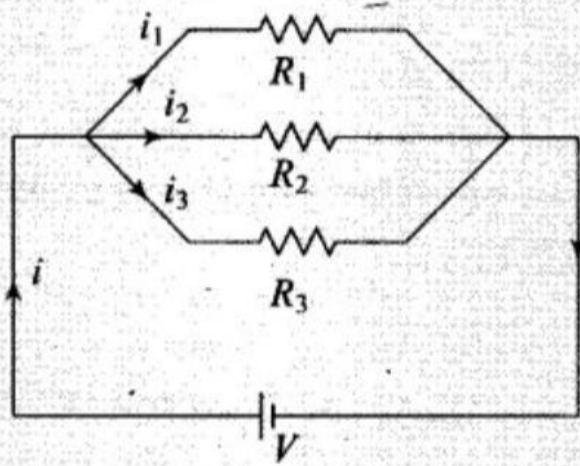

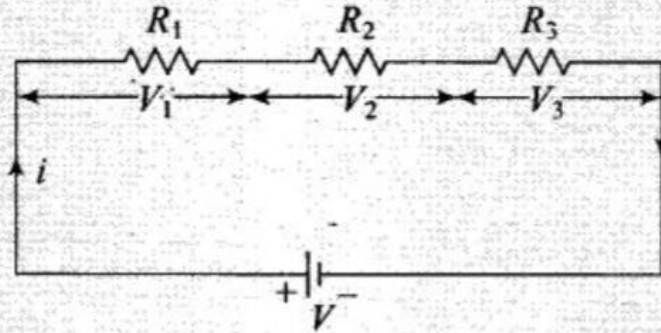Series grouping: Same current flows through each resistance but potential difference distributes in the ratio of resistance, i.e. $V \propto R$



In parallel combination: When all resistances are connected in parallel, the equivalent resistance R_p is given by

$$\frac{1}{R_p} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$

On multiplying both sides by R_{\min} , we have

$$\frac{R_{\min}}{R_p} = \frac{R_{\min}}{R_1} + \frac{R_{\min}}{R_2} + \dots + \frac{R_{\min}}{R_n}$$

Here, in RHS, there exist one term $\frac{R_{\min}}{R_{\min}} = 1$ and other terms are positive, so we have

$$\frac{R_{\min}}{R_p} = \frac{R_{\min}}{R_1} + \frac{R_{\min}}{R_2} + \dots + \frac{R_{\min}}{R_n} > 1$$

This shows that the resultant resistance $R_p < R_{\min}$.

Thus, in parallel combination, the equivalent resistance of resistors even less than the minimum resistance available in combination of resistors.

In series combination: When all resistances are connected in series, the equivalent resistance R_s is given by

$$R_s = R_1 + \dots + R_n$$

Here, in RHS, there exist one term having resistance R_{\max} .

So, we have

or $R_s = R_1 + \dots + R_{\max} \dots + \dots + R_n$


$$R_s = R_1 + \dots + R_{\max} \dots + R_n = R_{\max} + \dots (R_1 + \dots +) R_n$$

or $R_s \geq R_{\max}$


$$R_s = R_{\max}(R_1 + \dots + R_n)$$

Thus, in series combination, the equivalent resistance of resistors is greater than the maximum resistance available in combination of resistors.

Physical interpretation:

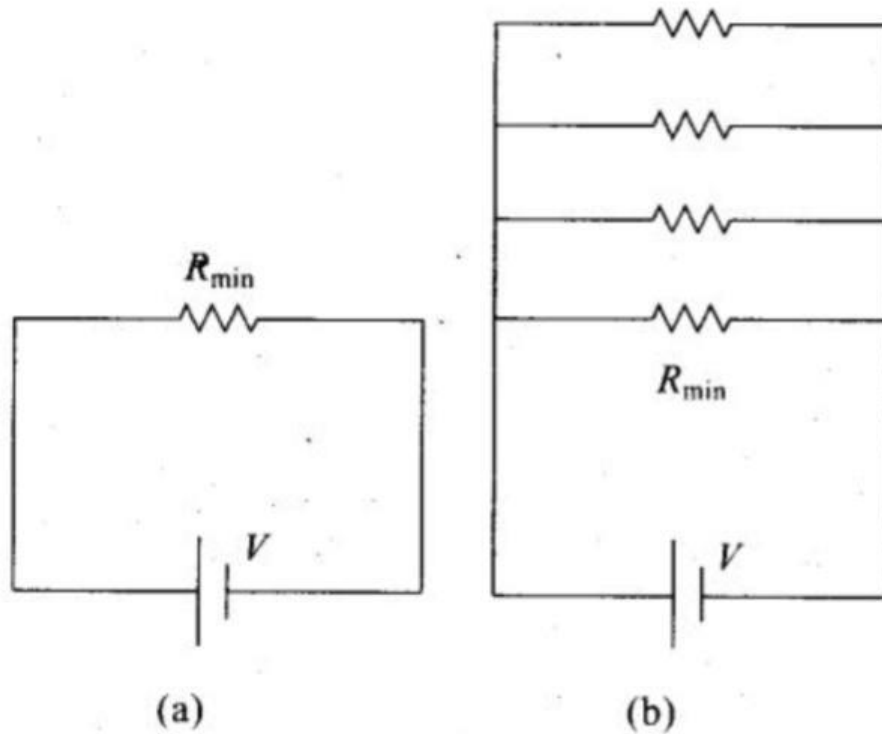

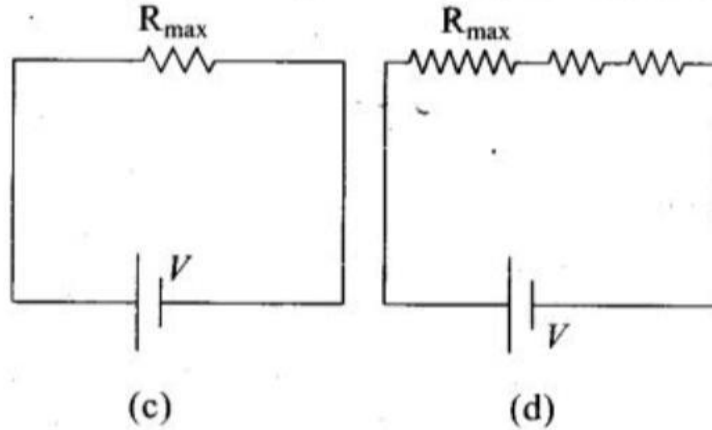In Fig. (b), R_{\min} provides an equivalent route as in Fig. (a) for current. But in addition there are $(n - 1)$ routes by the remaining $(n - 1)$ resistors. Current in Fig. (b) is greater than current in Fig. (a). Effective resistance in Fig. (b) $< R_{\min}$. Second circuit evidently affords a greater resistance.



In Fig. (d), R_{\max} provides an equivalent route as in Fig. (c) for current. Current in Fig. (d) $<$ current in Fig. (c). Effective resistance in Fig. (d) $> R_{\max}$. Second circuit evidently affords a greater resistance.