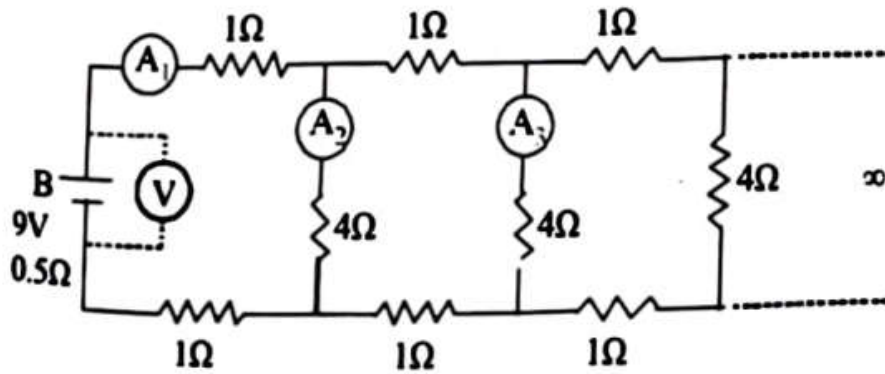


Q 01



A 9 V battery with internal resistance of 0.5Ω is connected across an infinite network as shown in the figure. All ammeters A_1, A_2, A_3 and voltmeter V are ideal.


Choose correct statement.

[Online April 8, 2017]

- (a) Reading of A_1 is 2 A (b) Reading of A_1 is 18 A
 (c) Reading of V is 9 V (d) Reading of V is 7 V

answer

(a) The given circuit can be redrawn as,

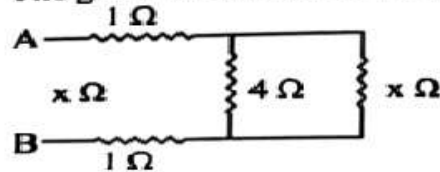

as 4Ω and $x \Omega$ are parallel $x' = \frac{1}{4} + \frac{1}{x} = \frac{(4+x)}{4x}$

$$x' = \frac{4x}{4+x}$$

& 1Ω and 1Ω are also parallel $x'' = 2 \Omega$

Now equivalent resistance of circuit

$$x = \frac{4x}{4+x} + 2 = \frac{8+6x}{4+x}$$

$$4x + x^2 = 8 + 6x$$

$$x^2 - 2x - 8 = 0$$

$$x = \frac{2 \pm \sqrt{4 - 4(1)(-8)}}{2} = \frac{2 \pm \sqrt{36}}{2} = \frac{2 \pm 6}{2} = 4 \Omega$$

$$\text{Reading of Ammeter } A_1 = \frac{V}{(R+r)}$$

$$A_1 = \frac{9}{4+0.5} = 2 \text{ Ampere}$$