

Q.01

(a) Three resistors $1\ \Omega$, $2\ \Omega$, and $3\ \Omega$ are combined in series. What is the total resistance of the combination?

(b) If the combination is connected to a battery of emf $12\ \text{V}$ and negligible internal resistance, obtain the potential drop across each resistor.

Answer

(a) Three resistors of resistances $1\ \Omega$, $2\ \Omega$, and $3\ \Omega$ are combined in series. Total resistance of the combination is given by the algebraic sum of individual resistances.

$$\text{Total resistance} = 1 + 2 + 3 = 6\ \Omega$$

(b) Current flowing through the circuit = I

Emf of the battery, $E = 12\ \text{V}$

Total resistance of the circuit, $R = 6\ \Omega$

The relation for current using Ohm's law is,

$$\begin{aligned} I &= \frac{E}{R} \\ &= \frac{12}{6} = 2\ \text{A} \end{aligned}$$

Potential drop across 1 Ω resistor = V_1

From Ohm's law, the value of V_1 can be obtained as

$$V_1 = 2 \times 1 = 2 \text{ V ... (i)}$$

Potential drop across 2 Ω resistor = V_2

Again, from Ohm's law, the value of V_2 can be obtained as

$$V_2 = 2 \times 2 = 4 \text{ V ... (ii)}$$

Potential drop across 3 Ω resistor = V_3

Again, from Ohm's law, the value of V_3 can be obtained as

$$V_3 = 2 \times 3 = 6 \text{ V ... (iii)}$$

Therefore, the potential drop across 1 Ω , 2 Ω , and 3 Ω resistors are 2 V, 4 V, and 6 V respectively.