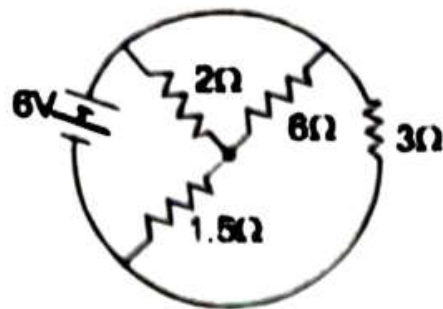


Q 06

The total current supplied to the circuit by the battery is



(a) 4 A

(b) 2 A

[2004]

(c) 1 A

(d) 6 A

ans

