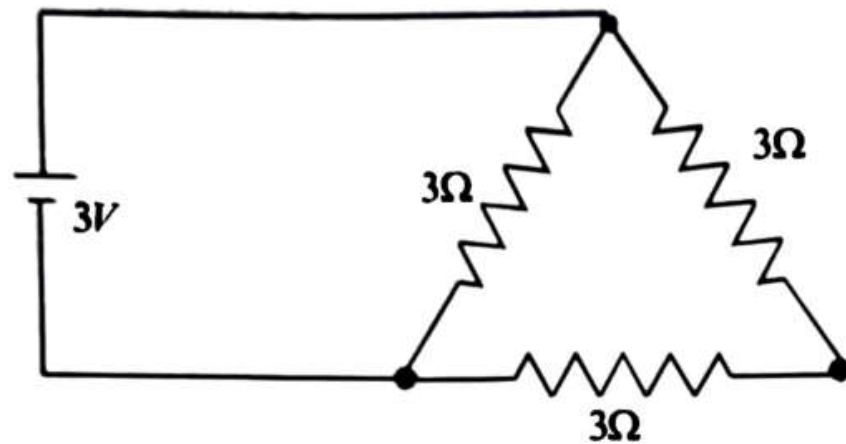


Q 08

A 3 volt battery with negligible internal resistance is connected in a circuit as shown in the figure. The current I , in the circuit will be [2003]



- (a) 1 A (b) 1.5 A (c) 2 A (d) 1/3 A

ans

$$(b) R_p = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$

$$\therefore V = IR \Rightarrow I = \frac{V}{R} = \frac{3}{2} = 1.5A$$

