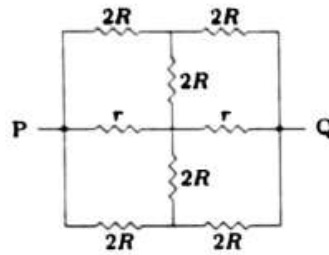



Q 11

The effective resistance between points P and Q of the electrical circuit shown in the figure is (2002)



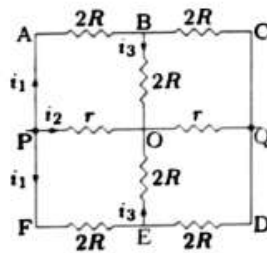- (A) $\frac{2Rr}{R+r}$ (B) $\frac{8R(R+r)}{3R+r}$ (C) $2r + 4R$ (D) $\frac{5R}{2} + 2r$

Sol. The given circuit is a good example of symmetry. When looking from P , branch PAB looks same as the branch PFE and hence the same current i_1 should flow through these branches.



Similarly, when looking from O , branches OB and OE look identical and same current i_3 should flow through them. Branches through P and Q are also identical. Apply Kirchoff's law in loop $ABOPA$ and $BCQOB$ to get

$$2Ri_1 + 2Ri_3 - i_2r = 0, \quad (1)$$

$$2R(i_1 - i_3) - r(i_2 + 2i_3) - 2Ri_3 = 0. \quad (2)$$

Solve equations (1) and (2) to get $i_3 = 0$ i.e., no current flows in the branch OB and OE . Hence, branch OB and OE can be removed from the circuit without affecting the effective resistance.

Thus, effective resistance of the circuit is $R_e = (4R \parallel 4R) \parallel 2r = \frac{2Rr}{R+r}$. We encourage you to exploit the symmetry to check that $i_3 = 0$.

Ans. A \square