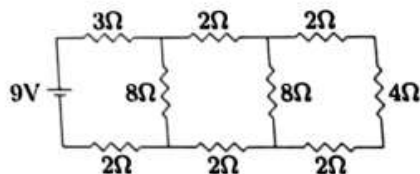



# Q 12

In the circuit shown in the figure, the current through (1998)



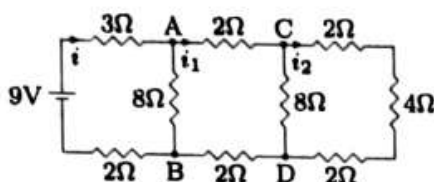- (A) the  $3\ \Omega$  resistor is  $0.50\ \text{A}$
- (B) the  $3\ \Omega$  resistor is  $0.25\ \text{A}$
- (C) the  $4\ \Omega$  resistor is  $0.50\ \text{A}$
- (D) the  $4\ \Omega$  resistor is  $0.25\ \text{A}$

**Sol.** Let  $R_1$  and  $R_2$  be the effective resistances of the circuits to the right of CD and AB, respectively (see figure). These resistances are given by  $R_1 = 2 + 4 + 2 = 8\ \Omega$  and  $R_2 = 2 + (8 \parallel R_1) + 2 = 2 + (8 \parallel 8) + 2 = 8\ \Omega$ .



Effective resistance of the complete circuit is  $R = 3 + (8 \parallel R_2) + 2 = 3 + (8 \parallel 8) + 2 = 9\ \Omega$ . Thus the current in  $3\ \Omega$  resistor is  $i = V/R = 9/9 = 1\ \text{A}$ . Current  $i$  is equally divided at node A giving  $i_1 = 0.5\ \text{A}$ . Current  $i_1$  is further divided into two equal parts at node C giving  $i_2 = 0.25\ \text{A}$ , the current through  $4\ \Omega$  resistor.

Ans. D  $\square$