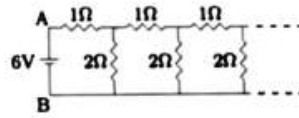



Q 13

An infinite ladder network of resistances is constructed with $1\ \Omega$ and $2\ \Omega$ resistances (see figure). The $6\ \text{V}$ battery between A and B has negligible internal resistance. (1987)



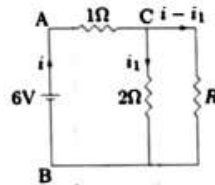- (a) Show that the effective resistance between A and B is $2\ \Omega$.
 (b) What is the current that passes through the $2\ \Omega$ resistance nearest to the battery?

Sol. Let the effective resistance between A and B be R . The ladder network consists of infinite number of units, where each unit consists of two resistances of values $R_1 = 1\ \Omega$ and $R_2 = 2\ \Omega$. The effective resistance of the ladder will not change by removal of one unit, say the unit close to the battery.



Thus, the effective resistance between A and B is equal to the resistance of the circuit shown in the figure i.e.,

$$R = R_1 + (R_2 \parallel R)$$

$$= R_1 + \frac{R_2 R}{R_2 + R} = 1 + \frac{2R}{2 + R}$$

Solve to get $R = 2\ \Omega$.

The effective resistance between A and B is $R = 2\ \Omega$. Thus, the current through the battery of $emf\ E =$

$6\ \text{V}$ is $i = E/R = 6/2 = 3\ \text{A}$. Since $R_2 = R = 2\ \Omega$, current i is equally divided at the node C giving $i_1 = i/2 = 1.5\ \text{A}$.

Ans. (b) $1.5\ \text{A}$ \square