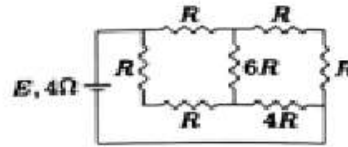


A battery of internal resistance $4\ \Omega$ is connected to the network resistances as shown in the figure. In order that the maximum power can be delivered to the network, the value of R (in Ω) should be


(1995)

Q 14



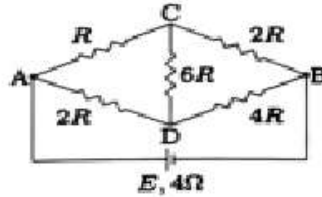- (A) $4/9$ (B) 2 (C) $8/3$ (D) 18

Sol. Given circuit forms a balanced Wheatstone bridge.



Thus, the resistance $6R$ in branch CD can be removed. Equivalent resistance between the nodes A and B is $R_e = (R + 2R) \parallel (2R + 4R) = 3R \parallel 6R = 2R$. The current through the circuit is $i = \frac{E}{R_e + r} = \frac{E}{3R + 4}$ and the power delivered to the network is

$$P = i^2 R_e = \frac{E^2}{2} \frac{R}{(R + 2)^2}$$

The power attains its maxima when

$$\frac{dP}{dR} = \frac{E^2}{2} \frac{(2 - R)}{(R + 2)^3} = 0,$$

which gives $R = 2\ \Omega$. Note that the power delivered by the battery is maximum when the load resistance (R_e) is equal to the internal resistance of the battery.

Ans. B \square