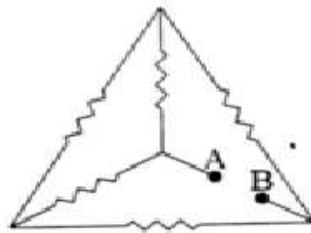
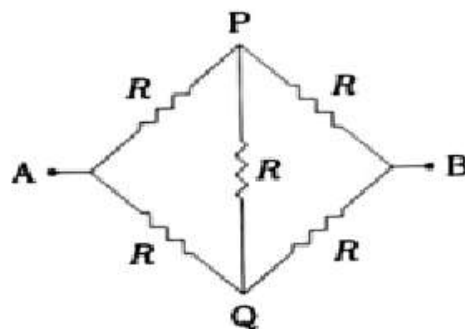


## Q 19

If each of the resistances in the network shown in the figure is  $R$ , what is the resistance between the terminals  $A$  and  $B$ ? (1978)



**Sol.** Given circuit is redrawn in the figure after moving out the terminals  $A$  and  $B$  from inside the triangle.



It is a balanced Wheatstone bridge. Hence, resistance in the branch  $PQ$  can be removed without affecting the effective resistance of the circuit. Hence, the

circuit has two branches,  $APB$  and  $AQB$ , each of resistance  $2R$ , connected in parallel. Thus, the effective resistance between  $A$  and  $B$  is

$$R_{AB} = (2R) \parallel (2R) = R.$$

**Ans.**  $R$   $\square$